



KOM3560

INDUSTRIAL ELECTRONICS


Spring : 2023

Lecture 4

DC Choppers – DC 2 DC Converters



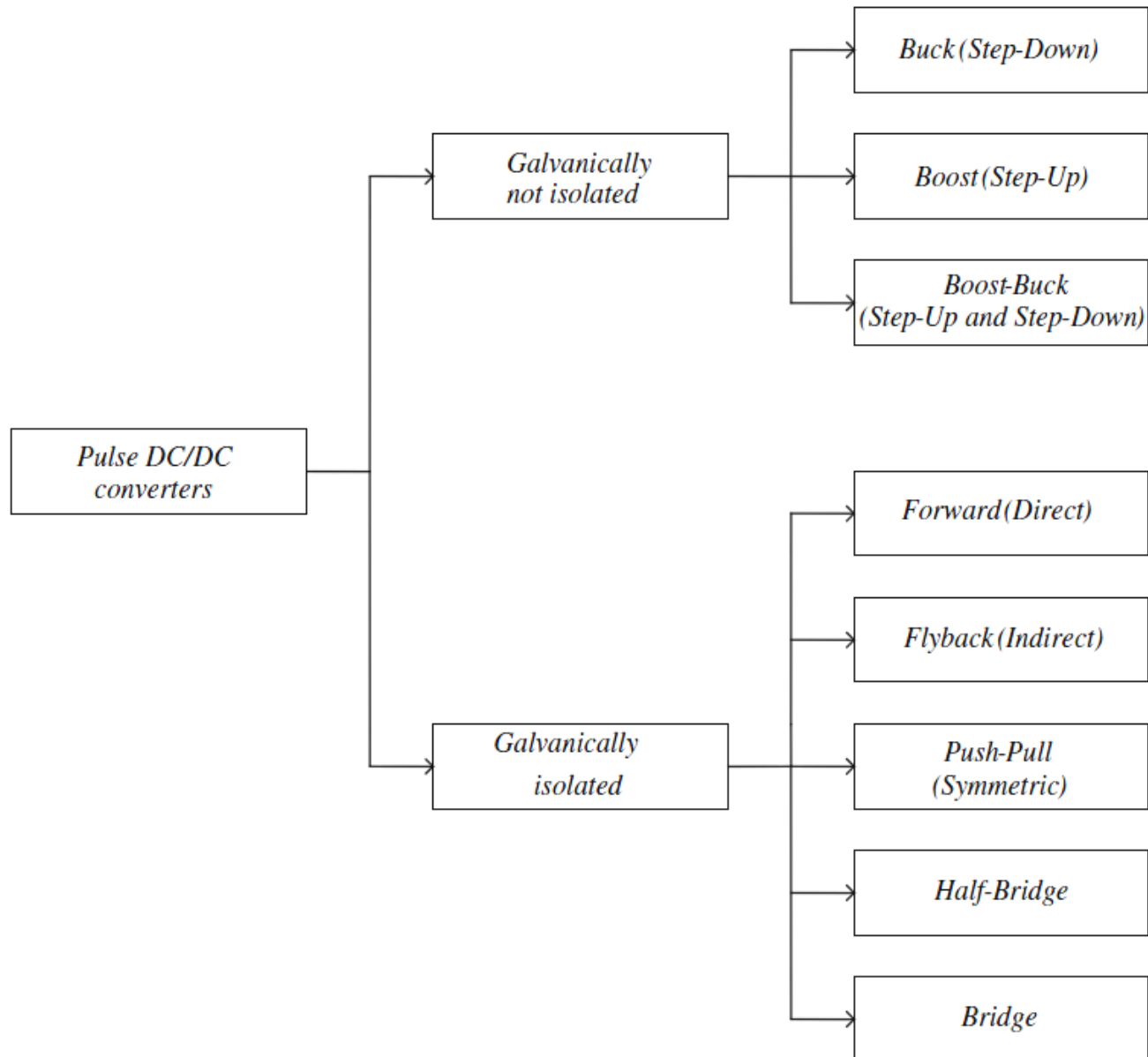Classification of pulse DC/DC converters according to the topology of the basic circuit;



THE BUCK (STEP-DOWN) CONVERTER


$$\lambda = \frac{T_1}{T_P} = \frac{I_T}{I_L}, \quad f_p = \frac{1}{T_P}$$

$$T_1 = \lambda T_P, \quad T_2 = (1 - \lambda) T_P$$

$$I_T = \lambda I_L, \quad I_D = (1 - \lambda) I_L$$

f_p : Anahtarlama (Darbe) Frekansı

λ : Bağlı İletim Süresi

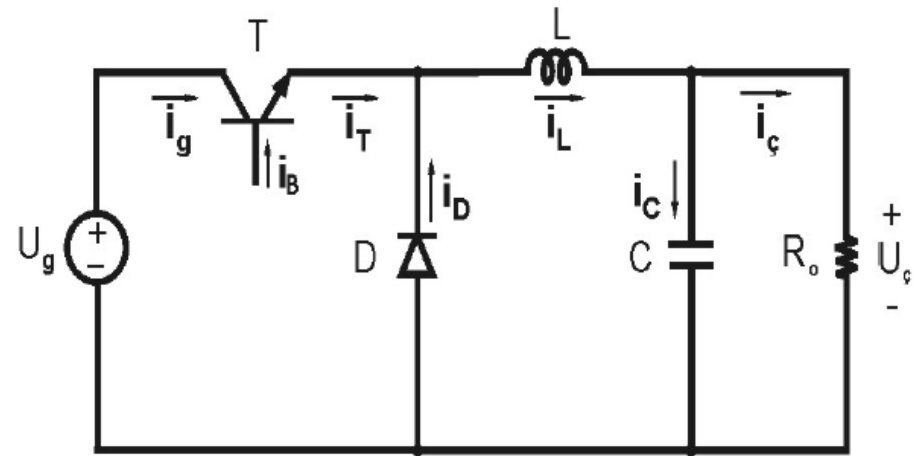

i_L : Sürekli, kesintisiz

$U_g, U_ç$ ve $I_ç$: Sabit

Assumptions

$\lambda = 2/3$ için,

U_g ve $I_ç$: 3 birim


$U_ç$ ve I_g : 2 birim

$$I_L = I_ç$$

$$U_ç = \lambda U_g$$


$$I_g = \lambda I_ç$$

General definitions

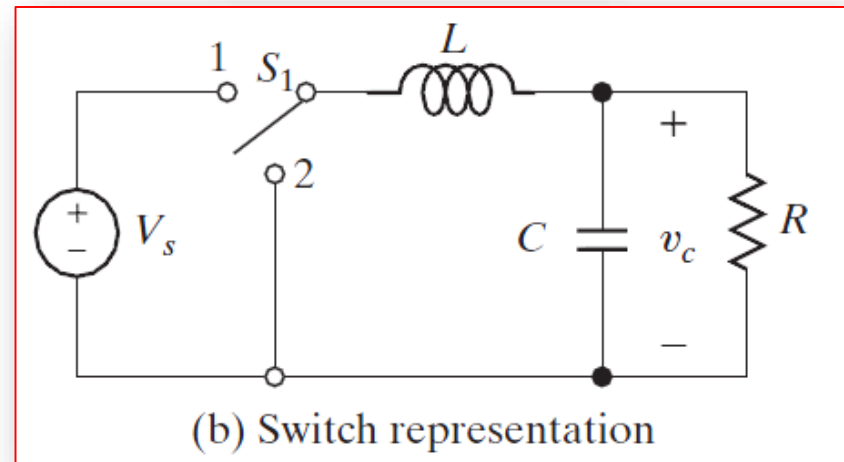

THE BOOST CONVERTER

$\lambda=2/3$ için Temel Dalga Şekilleri

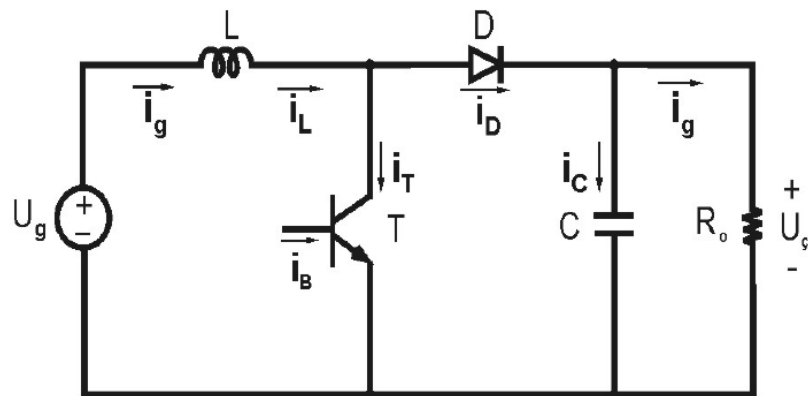

Output voltage


Input current

$$U_{\varphi} = \frac{1}{1-\lambda} U_g$$


$$I_g = \frac{1}{1-\lambda} I_{\varphi}$$

$$\Delta I_{L\max} = \frac{V_{\varphi}}{4f_p L}$$

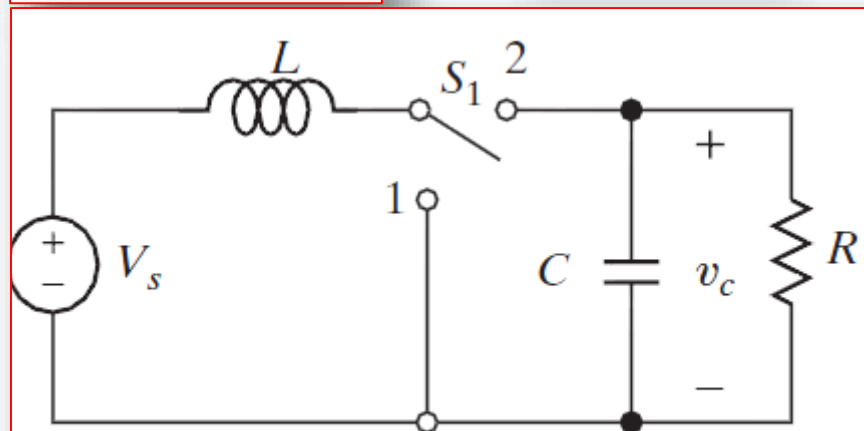
$$\Delta V_C = \frac{\lambda I_{\varphi}}{f_p C}$$



(b) Switch representation

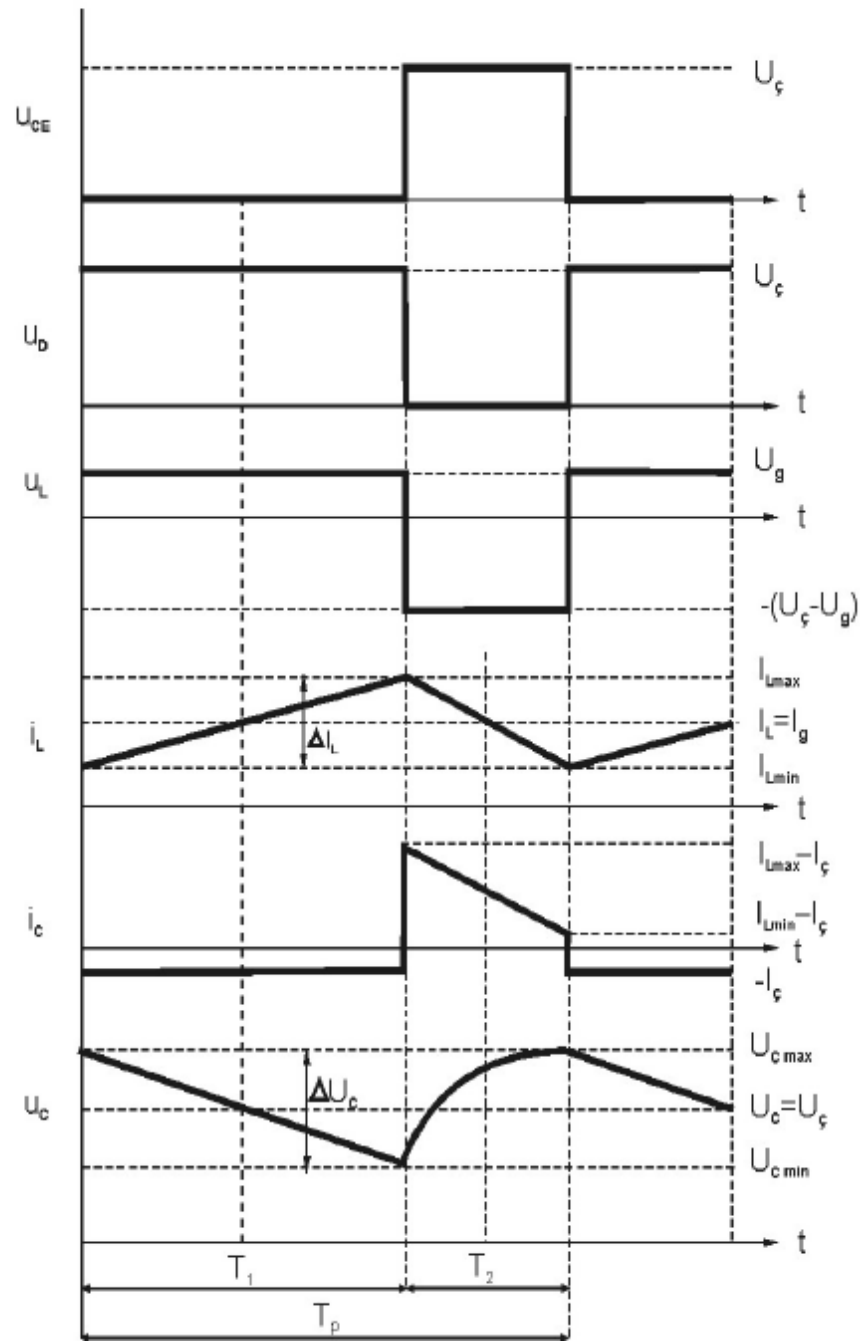

THE BUCK-BOOST CONVERTER

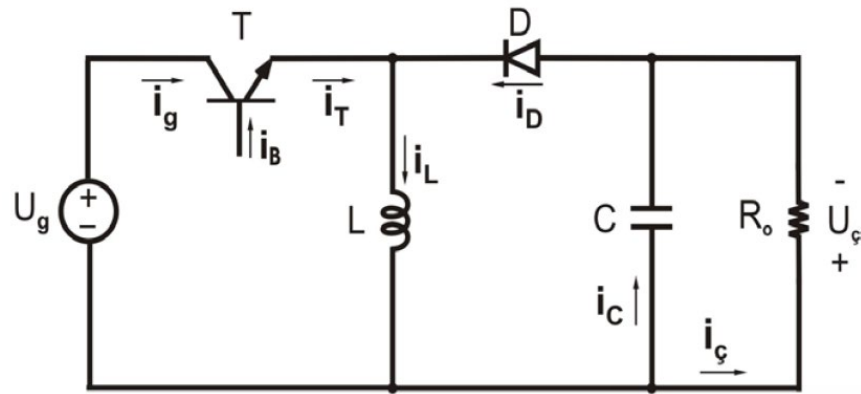


Assumptions

i_L : Sürekli, kesintisiz
 $U_g, U_φ$ ve $I_φ$: Sabit


$$I_L = I_g + I_φ$$

$$U_φ = \frac{\lambda}{1-\lambda} U_g$$

$$I_g = \frac{\lambda}{1-\lambda} I_φ$$

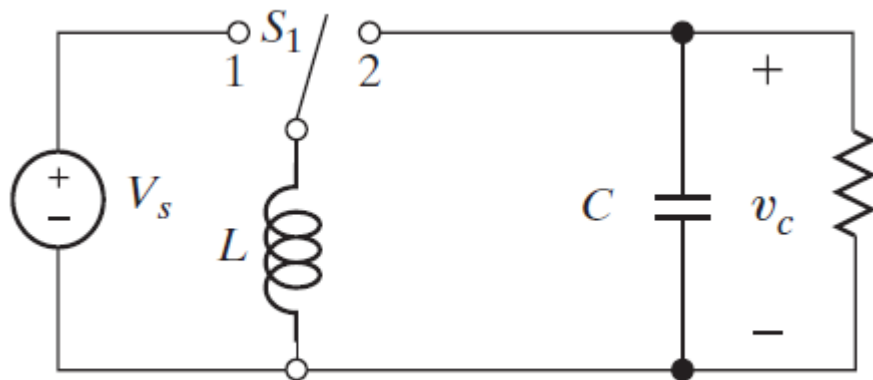

(b) Switch representation

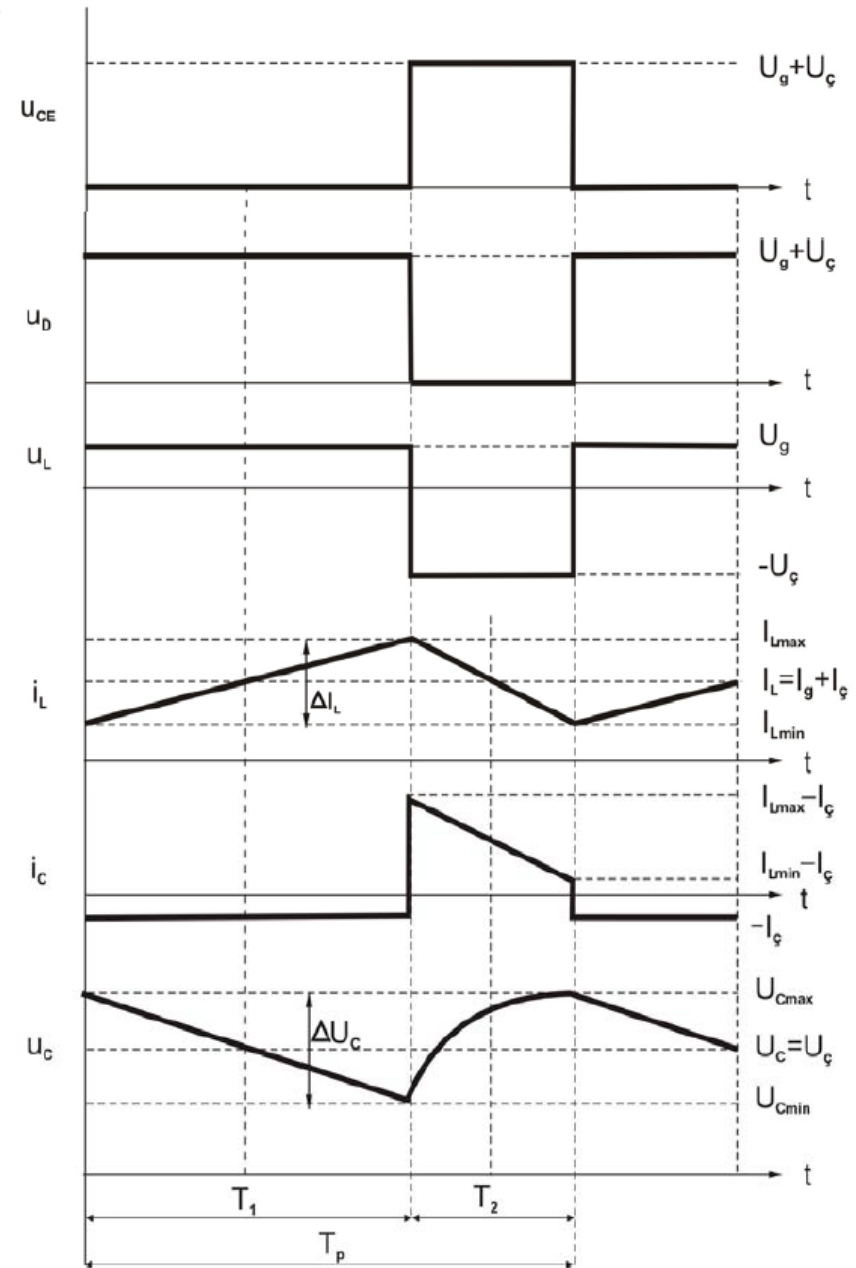

THE COMPARISON of BUCK BOOST CONVERTERs

Karşılaştırma Konusu	Düşürücü	Yükseltici	Düşürücü - Yükseltici
T₁ aralığında çalışma	V _i çıkışı besler. V _i , L'ye ilave bir enerji enjekte eder.	V _i , L'ye ilave bir enerji enjekte eder. C yükü besler.	V _i , L'ye ilave bir enerji enjekte eder. C yükü besler.
T₂ aralığında çalışma	L'deki ilave enerji çıkışa aktarılır.	V _i çıkışı besler. L'deki ilave enerji çıkışa aktarılır.	L'deki ilave enerji çıkışa aktarılır.
V_o çıkış gerilimi	λV_i	$\frac{1}{1-\lambda} V_i$	$\frac{\lambda}{1-\lambda} V_i$
I_i giriş akımı	λI_o	$\frac{1}{1-\lambda} I_o$	$\frac{\lambda}{1-\lambda} I_o$
V_o kontrol aralığı	0 ile V _i	V _i ile V _{omax}	- (0 ile V _{omax})
Güç elemanlarının maruz kaldığı gerilim	V _i	V _o	V _i + V _o
I_L endüktans akımı	I _o	I _i	I _i + I _o
I_i'deki dalgalanma	Büyük	Çok küçük	Büyük
I_o'daki dalgalanma	Çok küçük	Büyük	Büyük
V_o'daki dalgalanma	Çok küçük	Büyük	Büyük
V_o'ın yönü	Pozitif	Pozitif	Negatif
Boşta çalışma özelliği	Var	Yok	Yok

Example:


Consider a buck converter with the following circuit parameters; $U_g = 30V$, $f = 50kHz$, $I_{\phi} = 1A$. Additionally, voltage drop across BJT and Diode in conduction mode are defined as $U_{CEsat} = 0,4V$ and $U_D = 0,6V$

- Derive the expression between the input and output currents in terms of duty cycle
- Sketch the inductance current and voltage respectively for $\lambda=1/2$ by ignoring voltage drop of power switching components and find the output voltage in terms of duty cycle and the input voltage
- Without ignoring voltage drop of power switching components perform (b) again
- Under ideal operating conditions, calculate duty cycle, input current and efficiency of the converter
- Under practical operating conditions including component losses, calculate duty cycle, input current and efficiency of the converter

Example:

buck converter with $U_g = 30V$, $f = 50kHz$, $I_\zeta = 1A$. $U_{CESat} = 0,4V$ and $U_D = 0,6V$

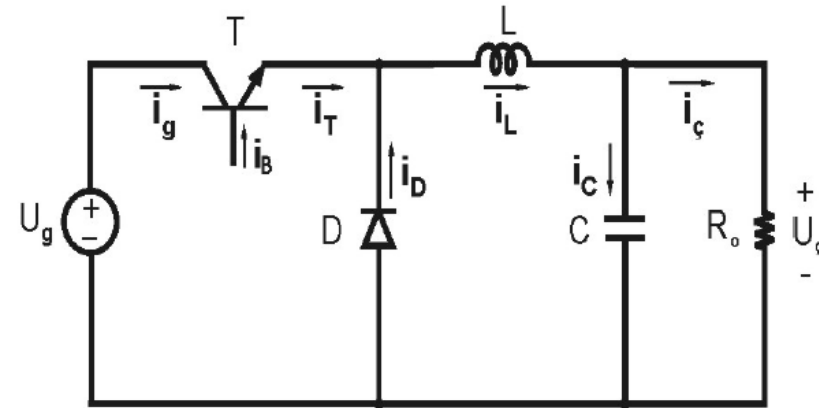a) Derive the expression between the input and output currents in terms of duty cycle



$$\begin{aligned} I_L &= I_T + I_D \\ I_T &= \lambda \cdot I_L \\ I_D &= (1 - \lambda) \cdot I_L \\ T_p &= T_1 + T_2 \\ T_1 &= \lambda \cdot T_p \\ T_2 &= (1 - \lambda) \cdot T_p \\ \lambda &= \frac{T_1}{T_p} = \frac{I_T}{I_L} \end{aligned}$$

General equations
for DC-DC
converters

For buck converter

$$\begin{aligned} I_L &= I_\zeta \\ I_T &= I_g \end{aligned}$$




$$\begin{aligned} I_L &= I_T + I_D \\ I_\zeta &= I_g + (1 - \lambda) \cdot I_\zeta \\ I_\zeta &= I_\zeta - \lambda \cdot I_\zeta - I_\zeta \\ I_g &= \lambda \cdot I_\zeta \end{aligned}$$

Example:

buck converter with $U_g = 30V$, $f = 50kHz$, $I_\zeta = 1A$. $U_{CEsat} = 0,4V$ and $U_D = 0,6V$

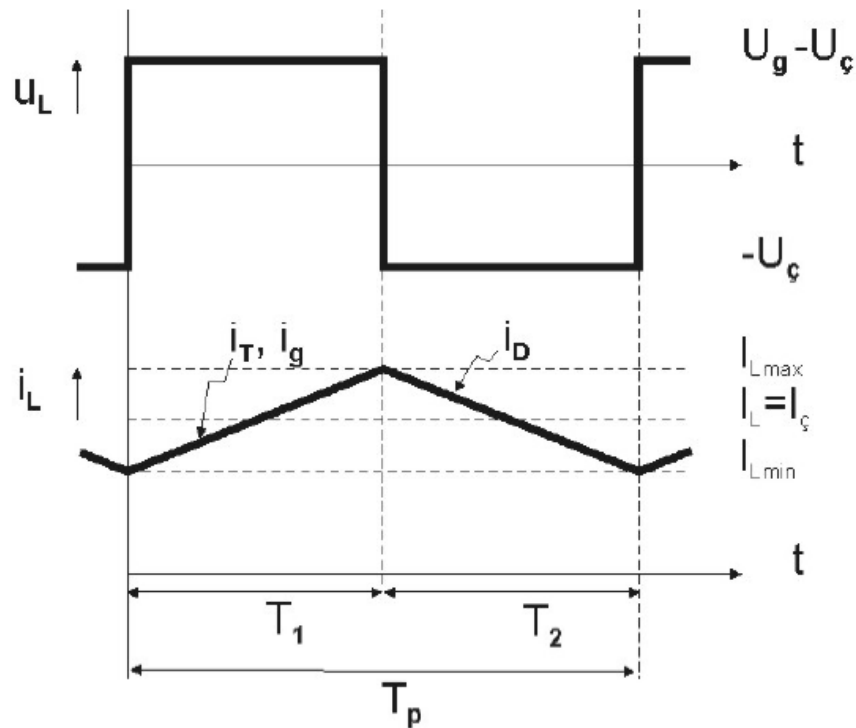- a) Sketch the inductance current and voltage respectively for $\lambda=1/2$ by ignoring voltage drop of power switching components and find the output voltage in terms of duty cycle and the input voltage



From the equality of (+) and (-) wave form

$$T_1(U_g - U_\zeta) = T_2 U_\zeta$$

$$\lambda T_p (U_g - U_\zeta) = (1 - \lambda) T_p U_\zeta$$


$$\lambda U_g - \lambda U_\zeta = U_\zeta - \lambda U_\zeta$$

$$U_\zeta = \lambda U_g$$

Example:

buck converter with $U_g = 30V$, $f = 50kHz$, $I_\zeta = 1A$. $U_{CEsat} = 0,4V$ and $U_D = 0,6V$

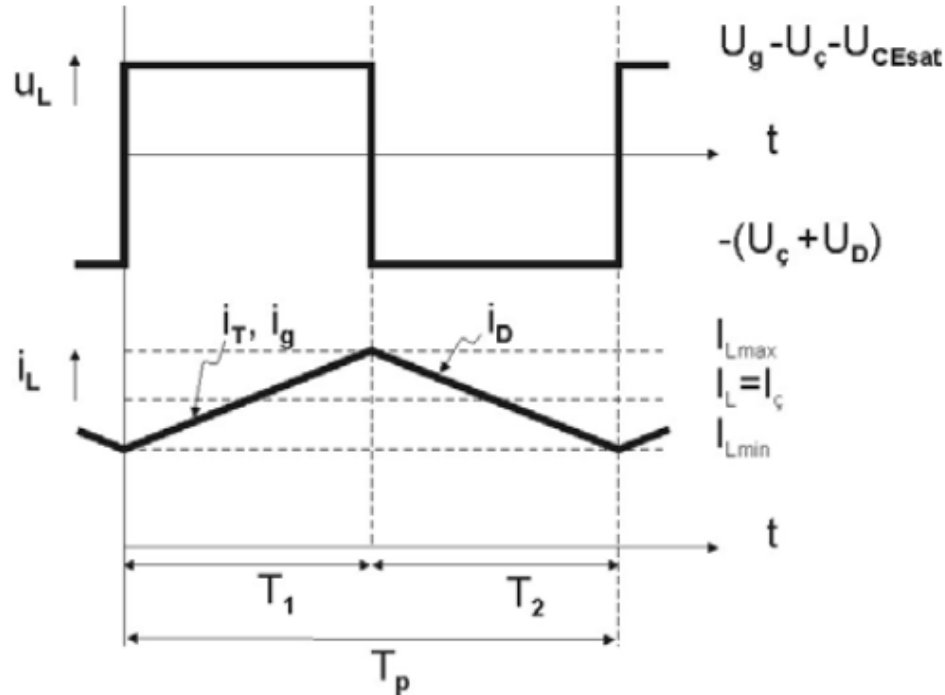a) Without ignoring voltage drop of power switching components perform (b) again



From the equality of (+) and (-) wave form



$$T_1(U_g - U_\zeta - U_{CEsat}) = T_2(U_\zeta + U_D)$$

$$\lambda U_g - \lambda U_\zeta - \lambda U_{CEsat} = U_\zeta + U_D - \lambda U_\zeta - \lambda U_D$$

$$U_\zeta = \lambda(U_g - U_{CEsat} + U_D) - U_D$$

Example:

buck converter with $U_g = 30V$, $f = 50kHz$, $I_\zeta = 1A$. $U_{CEsat} = 0,4V$ and $U_D = 0,6V$

- a) Under ideal operating conditions, calculate duty cycle, input current and efficiency of the converter

$$U_\zeta = \lambda U_g$$

$$15 = \lambda 30$$

$$\lambda = 1/2$$

$$I_g = \lambda I_\zeta$$

$$I_g = \frac{1}{2} 1$$

$$I_g = 0,5 \text{ A}$$



$$\eta = \frac{P_\zeta}{P_g} = \frac{U_\zeta I_\zeta}{U_g I_g} = \frac{15 \cdot 1}{30 \cdot 0,5}$$

$$\eta = 1 \Rightarrow \%100$$

Example:

buck converter with $U_g = 30V$, $f = 50kHz$, $I_\zeta = 1A$. $U_{CEsat} = 0,4V$ and $U_D = 0,6V$

- a) Under practical operating conditions including component losses, calculate duty cycle, input current and efficiency of the converter

$$15 = \lambda(U_g - U_{CEsat} + U_D) - U_D$$

$$15 = \lambda(30 - 0,4 + 0,6) - 0,6$$

$$\Rightarrow \lambda \cong 0,517$$

$$I_g = \lambda I_\zeta$$

$$= 0,517 \cdot 1$$

$$I_g = 0,517 \text{ A}$$


$$\eta = \frac{P_\zeta}{P_g} = \frac{U_\zeta I_\zeta}{U_g I_g} = \frac{15 \cdot 1}{30 \cdot 0,517}$$

$$\eta \cong 0,967 \Rightarrow \%96,7$$

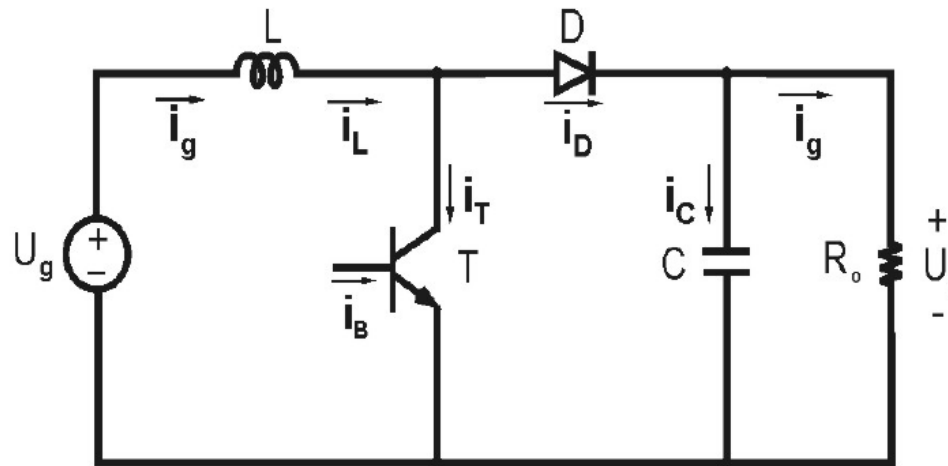Example:

Consider a boost converter with the following circuit parameters; $U_g = 12V$, $f = 100kHz$, $I_\zeta = 1A$ and $U_\zeta = 60$.

- Find the input current, currents flowing through the power switching devices and the duty cycle
- Find average value of the currents in conduction intervals of the power switching devices
- Determine the duty cycle value and corresponding input current
- Calculate the required inductance and capacitance values If 10% fluctuation in inductance current and 1% fluctuation in output voltage is allowed



Example:

Consider a boost converter with the following circuit parameters; $U_g = 12V$, $f = 100kHz$, $I_{\zeta} = 1A$ and $U_{\zeta} = 60$.

- a) Find the input current, currents flowing through the power switching devices and the duty cycle

If the losses on the components are ignored

$$P_g = P_{\zeta}$$

$$U_g \cdot I_g = U_{\zeta} \cdot I_{\zeta}$$

$$12 \cdot I_g = 60 \cdot 1$$

$$\Rightarrow I_g = 5 \text{ A}$$

In boost converter;

$$I_L = I_g \text{ ve } I_D = I_{\zeta}$$

$$I_L = I_g = 5 \text{ A}$$

$$I_D = I_{\zeta} = 1 \text{ A}$$

$$I_L = I_T + I_D$$

$$I_T = \lambda \cdot I_L$$

$$I_D = (1 - \lambda) \cdot I_L$$

$$T_p = T_1 + T_2$$

$$T_1 = \lambda \cdot T_p$$

$$T_2 = (1 - \lambda) \cdot T_p$$

$$\lambda = \frac{T_1}{T_p} = \frac{I_T}{I_L}$$

$$I_L = I_T + I_D$$

$$I_T = \lambda \cdot I_L$$

$$I_D = (1 - \lambda) \cdot I_L$$

$$I_L = I_T + I_D$$

$$5 = I_T + 1$$

$$\Rightarrow I_T = 4 \text{ A}$$

$$I_T = \lambda \cdot I_L$$

$$4 = \lambda \cdot 5$$

$$\Rightarrow \lambda = 4/5 = 0,8$$

Example:

Consider a boost converter with the following circuit parameters; $U_g = 12V$, $f = 100kHz$, $I_\zeta = 1A$ and $U_\zeta = 60$.

- a) Find average value of the currents in conduction intervals of the power switching devices

$$I_{T_{T1}} = I_{D_{T1}} = I_L \Rightarrow I_{T_{T1}} = I_{D_{T1}} = I_L = 5 \text{ A}$$

- b) Determine the duty cycle value and corresponding input current

$$U_\zeta = 60 \text{ V}$$

$$I_\zeta = 1 \text{ A}$$

$$U_g = 12 \text{ V}$$

$$U_\zeta = \frac{1}{1-\lambda} U_g$$

$$I_g = \frac{1}{1-\lambda} I_\zeta = \frac{1}{1-0,8} 1$$

$$I_g = 5 \text{ A}$$

$$60 = \frac{1}{1-\lambda} 12$$

$$60 - 60\lambda = 12$$

$$60\lambda = 48$$

$$\Rightarrow \lambda = \frac{48}{60} = \frac{4}{5} = 0,8$$

Example:

Consider a boost converter with the following circuit parameters; $U_g = 12V$, $f = 100kHz$, $I_c = 1A$ and $U_c = 60$.

- a) Calculate the required inductance and capacitance values If 10% fluctuation in inductance current and 1% fluctuation in output voltage is allowed

$$f_p = 100 \text{ kHz}$$

$$T_p = \frac{1}{f_p} = \frac{1}{100 \cdot 10^3}$$

$$T_p = 10 \text{ } \mu\text{s}$$

$$T_1 = \lambda \cdot T_p = 0,8 \cdot 10 \cdot 10^{-6}$$

$$T_1 = 8 \text{ } \mu\text{s}$$

$$\frac{\Delta I_L}{I_L} = \frac{10}{100} \text{ ve } \frac{\Delta U_c}{U_c} = \frac{1}{100}$$

$$\frac{\Delta I_L}{5} = \frac{10}{100}$$

$$\Rightarrow \Delta I_L = 0,5 \text{ A}$$

$$\frac{\Delta U_c}{U_c} = \frac{1}{100}$$

$$\Rightarrow \Delta U_c = 0,6 \text{ V}$$

$$\Delta I_L = \frac{U_g}{L} T_1$$

$$0,5 = \frac{12}{L} 8 \cdot 10^{-6}$$

$$\Rightarrow L = 192 \text{ } \mu\text{H}$$

$$C \cdot \Delta U_c = I_c \cdot \Delta t$$

$$C \cdot 0,6 = 1 \cdot 8 \cdot 10^{-6}$$

$$\Rightarrow C = 13,33 \text{ } \mu\text{F}$$

Electrical isolation requirement



- A basic disadvantage of the dc-dc converters (buck, boost etc.) is the electrical connection between the input and the output.
- If the input supply is grounded, that same ground will be present on the output.
- A way to isolate the output from the input electrically is with a transformer.
- If the dc-dc converter has a first stage that rectifies an ac power source to dc, a transformer could be used on the ac side.
- However, not all applications require ac to dc conversion as a first stage.
- Moreover, a transformer operating at a low frequency (50 or 60 Hz) requires a large magnetic core and is therefore relatively large, heavy, and expensive.

Electrical isolation requirement

- A more efficient method of providing electrical isolation between input and output of a dc-dc converter is to use a transformer in the switching scheme.
- The switching frequency is much greater than the ac power-source frequency, enabling the transformer to be small.
- Additionally, the transformer turns ratio provides increased design flexibility in the overall relationship between the input and the output of the converter.
- With the use of multiple transformer windings, switching converters can be designed to provide multiple output voltages.

2.08 Kilograms




0.080 kg




Electrical isolation requirement

(a) Transformer;

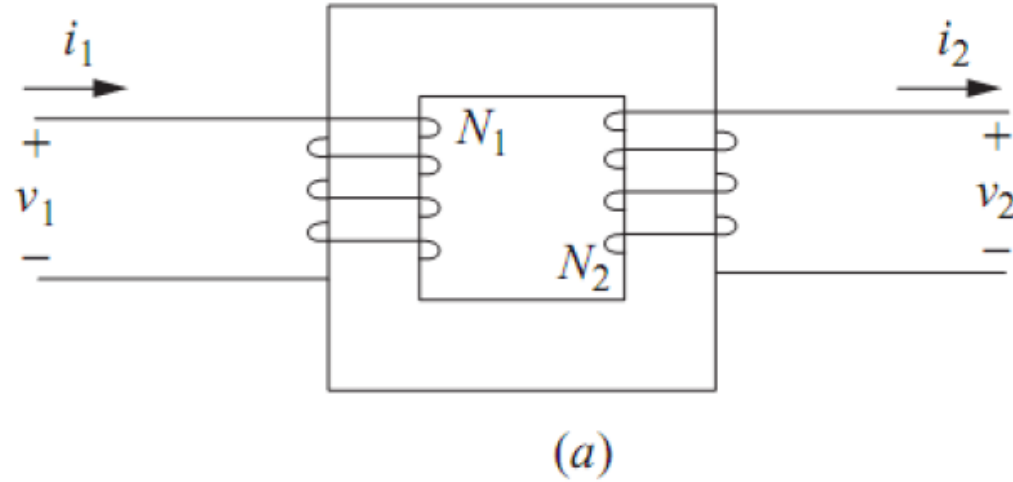


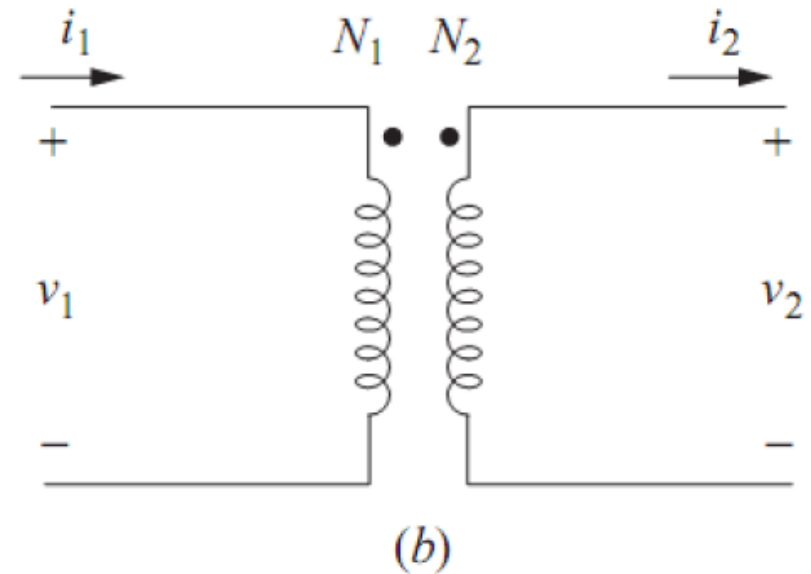(b) Ideal model

$$\frac{v_1}{v_2} = \frac{N_1}{N_2}$$
$$\frac{i_1}{i_2} = \frac{N_2}{N_1}$$



Electrical isolation requirement

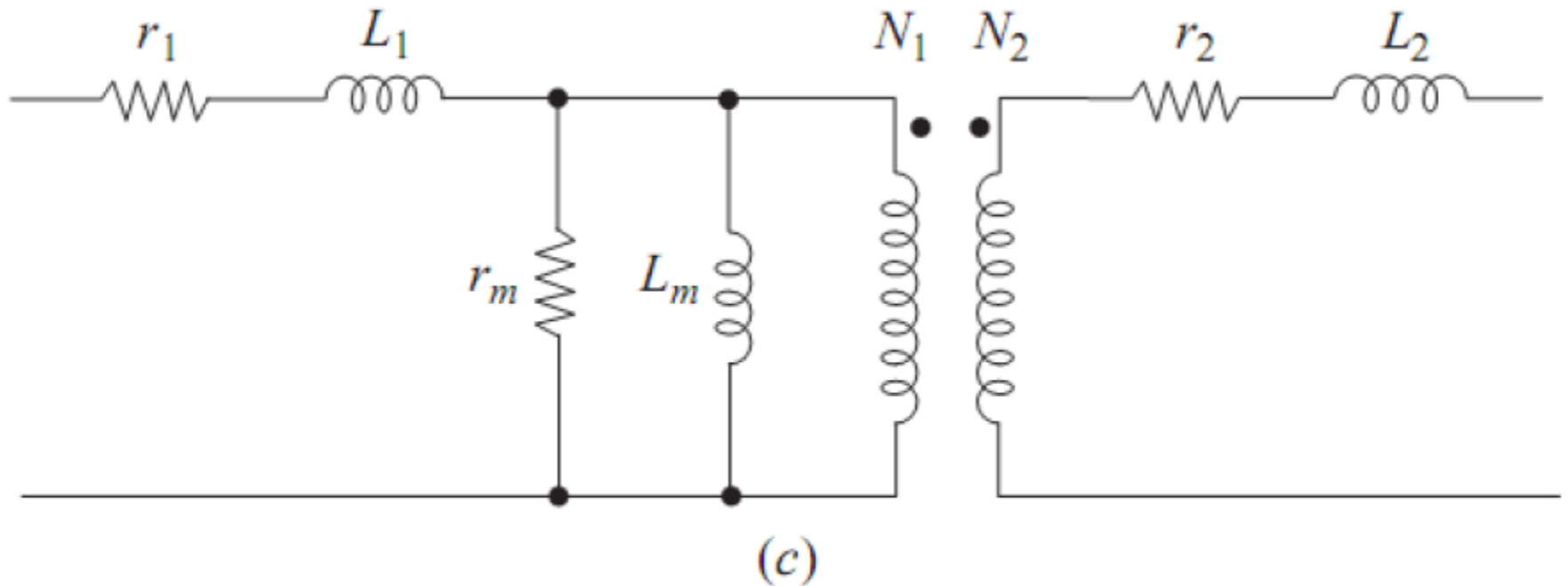


(c) Complete model


Electrical isolation requirement

The leakage inductances L_1 and L_2 are usually not crucial to the general operation of the power electronics circuits described in this chapter, but they are important when considering switching transients.

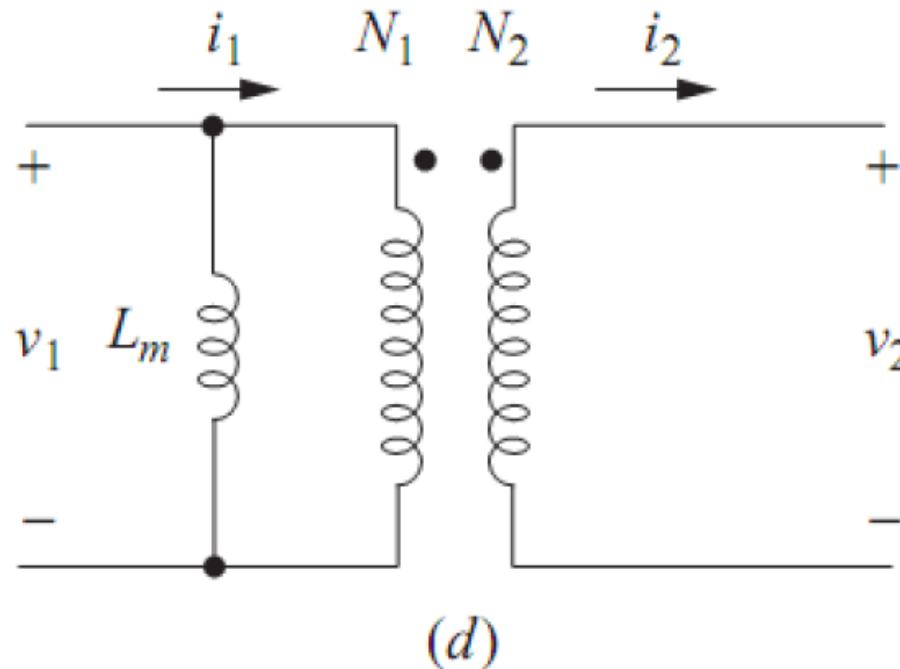Magnetic core reset is important! The average voltage of L_m must be zero! Otherwise the transformer saturates!




Electrical isolation requirement

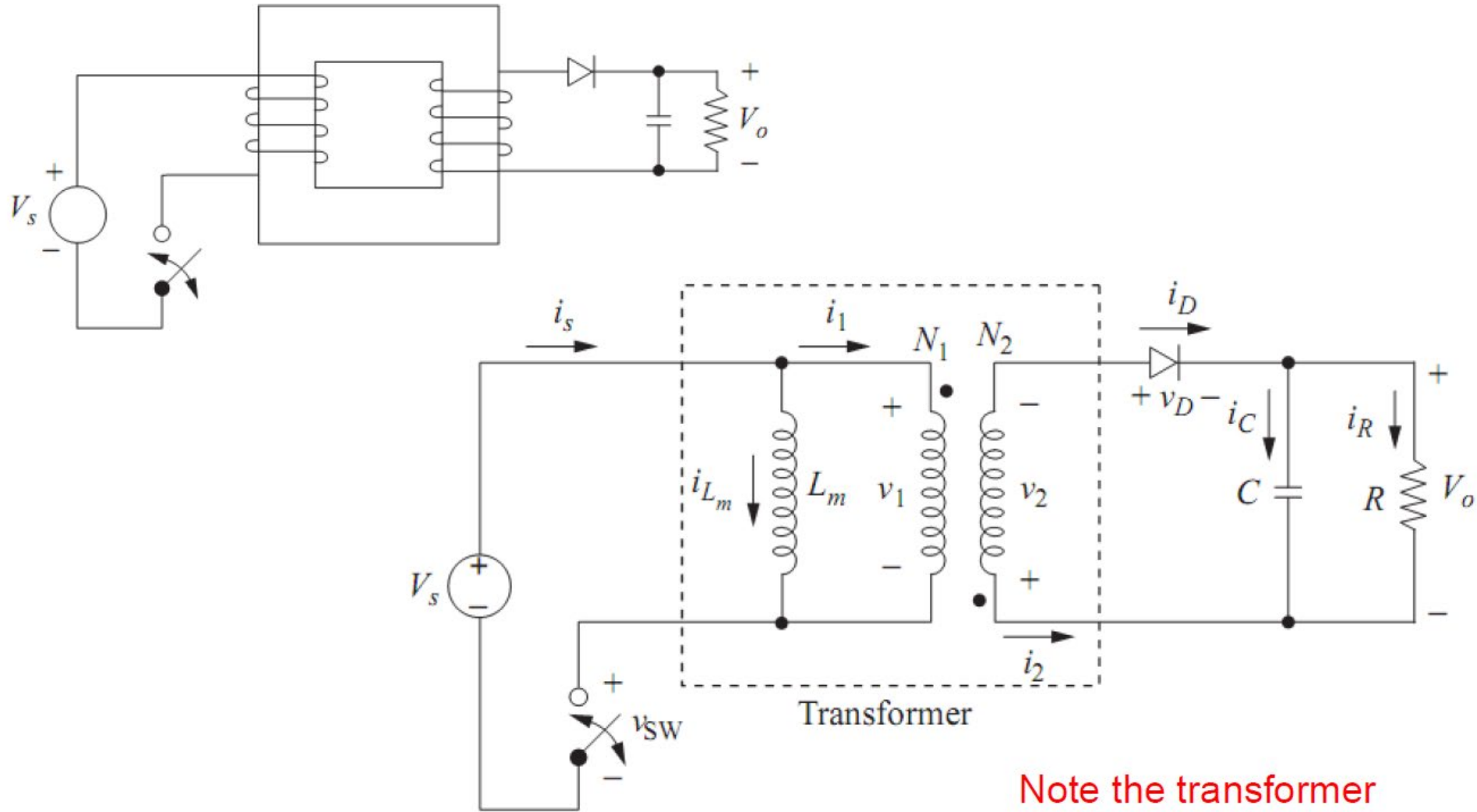

Note the transformer winding direction !!!

Electrical isolation requirement

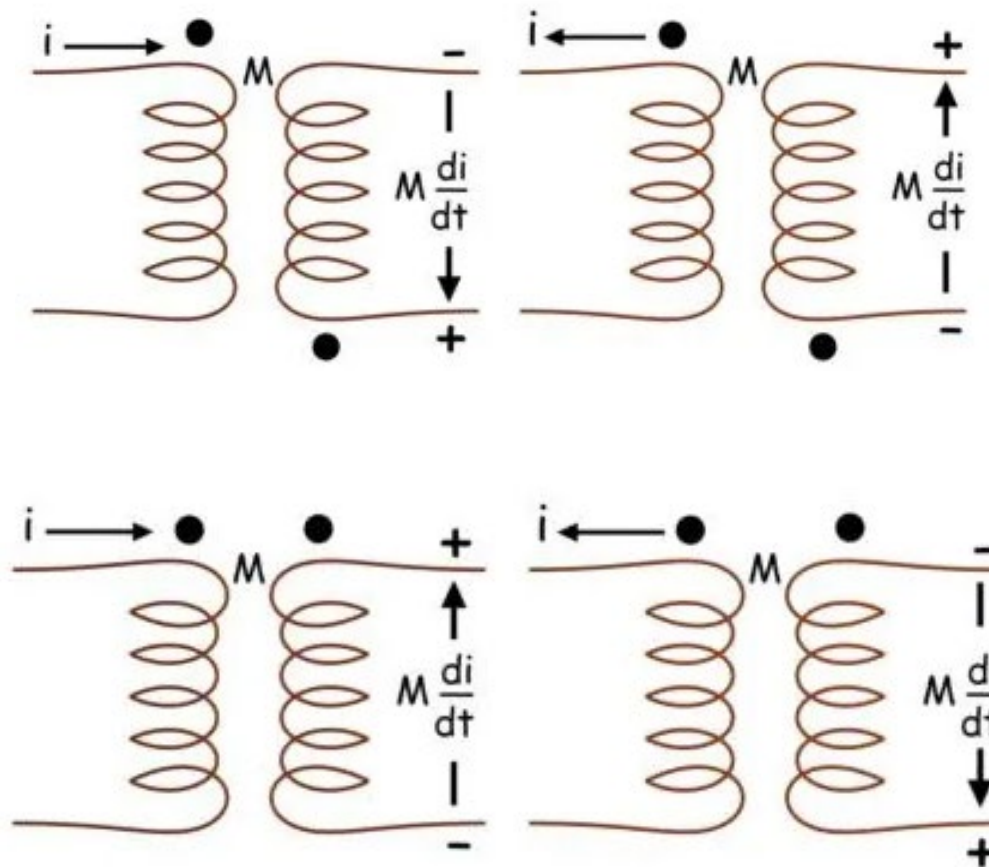
If at an instant, current is entering a coil through dotted end then mutually induced emf on the other coil will have the positive polarity at the dotted end of the later. It can be said in a different way that if the current is leaving a coil through the dotted end then mutually induced emf on the other coil will have the negative polarity at the dotted end of the later.



Electrical isolation requirement


Mutual inductance

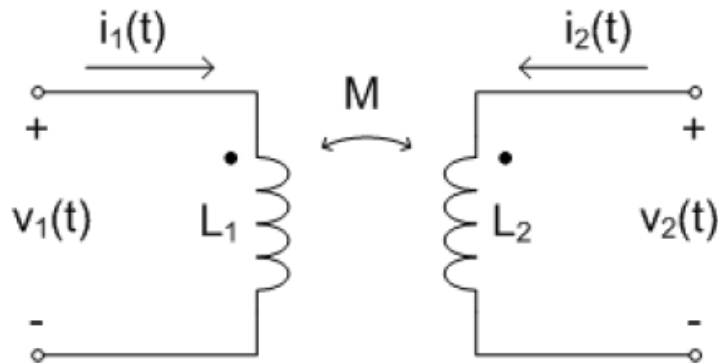- Property of electric circuits in which a time-varying current in one inductor results in a voltage across a second inductor
- Due to flux linkage between the two inductors
- Denoted as **M**
- Units: **Henries (H)**
- Dot convention** determines polarity of induced voltages:



$$v_1(t) = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$



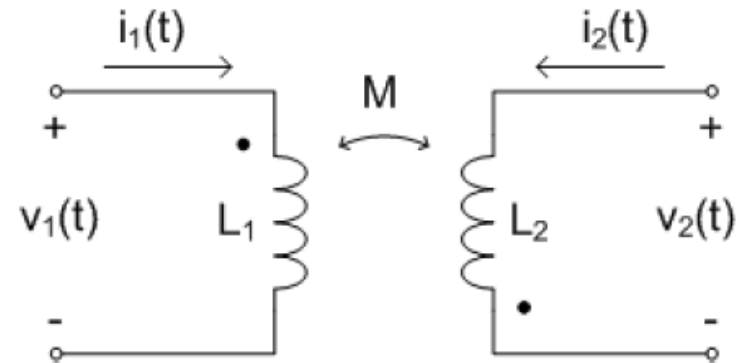
$$v_2(t) = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$



$$v_1(t) = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$v_2(t) = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$

Transformer Configurations

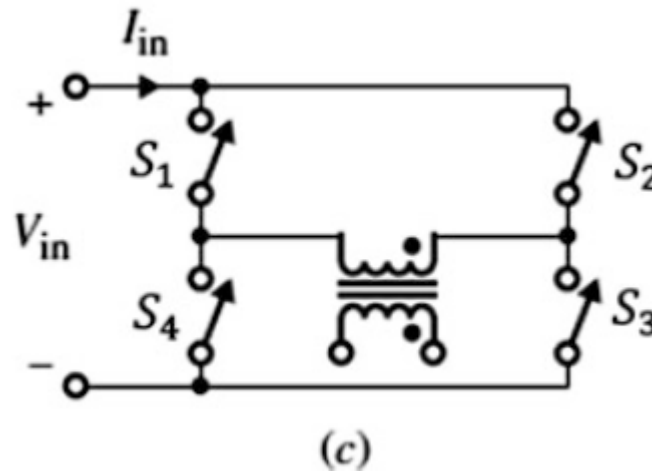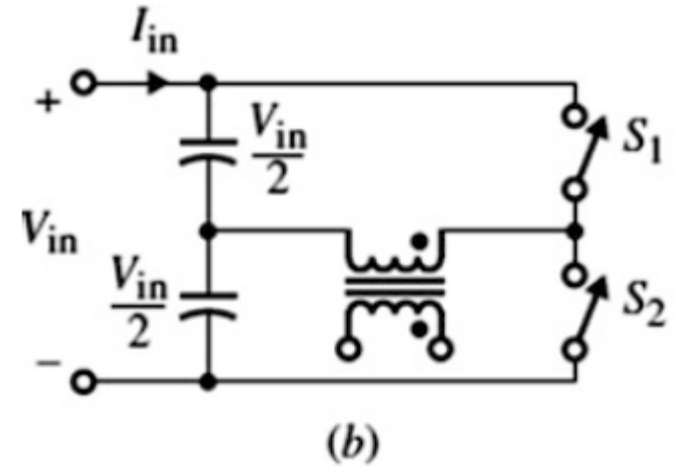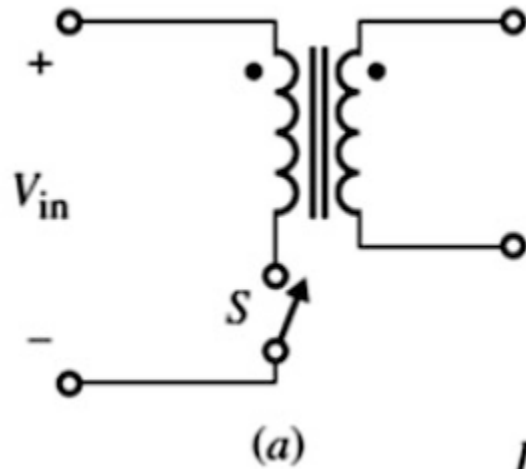


- (a) single-ended,
- (b) half-bridge,
- (c) full-bridge


These configurations are the most popular ones in today's switch-mode power supply design

Forward Converter

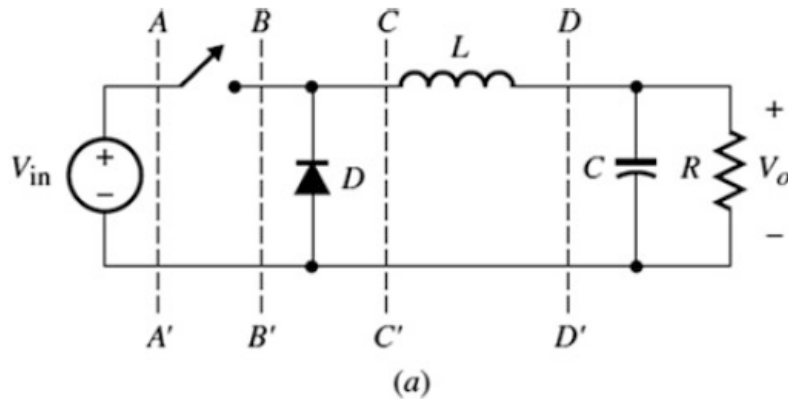Let us consider isolating the input and output voltages of the buck converter by inserting an ac transformer.




(a) Buck converter and

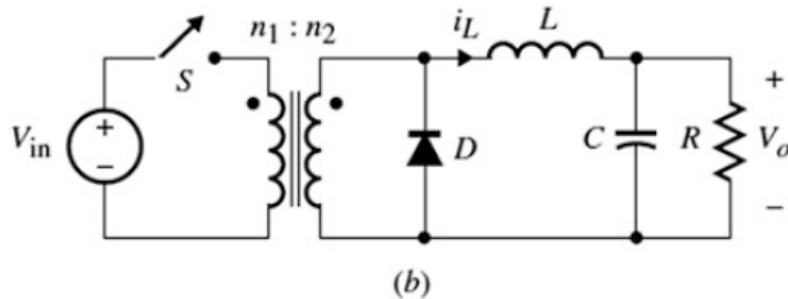

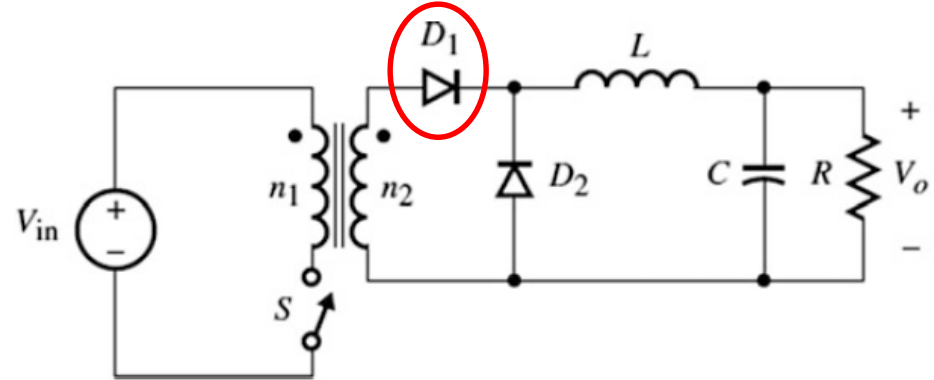(b) isolated buck converter

The term “forward” indicates that the energy from the source is directly forwarded to the load.


to avoid the problem of transformer saturation is to add another diode




Isolated buck-derived converter, known as single-ended forward converter

***This will not work properly since its magnetizing current will not be allowed to reset to zero, causing the magnetizing current to continuously increase linearly until it finally saturates the core. A more practical forward converter must include a transformer core resetting circuit as shown in next slide

Forward Converter

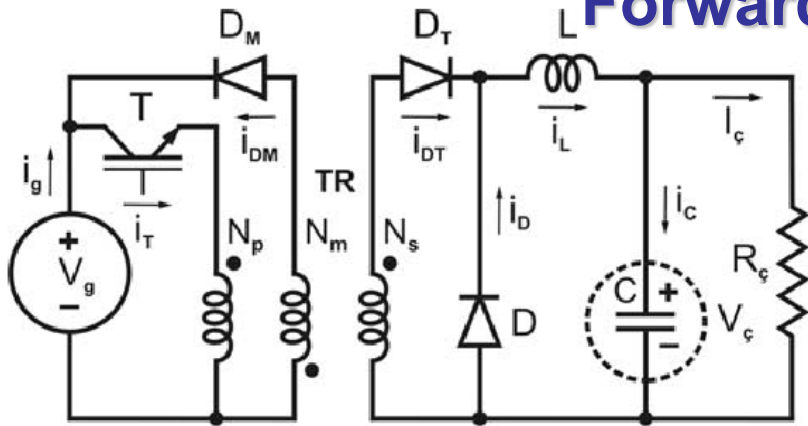
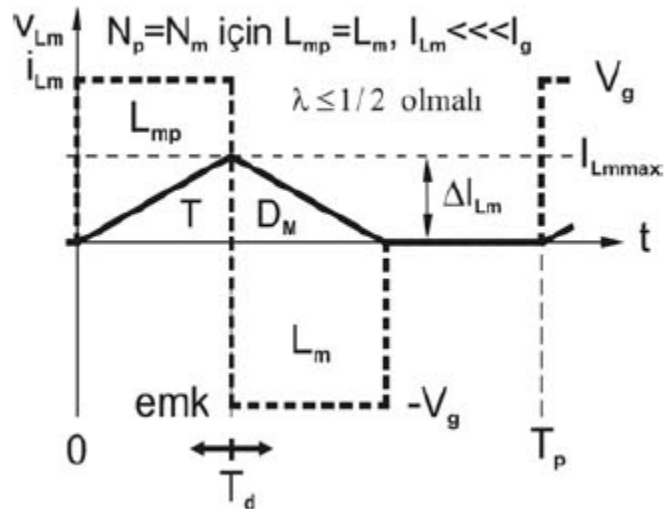
$$a = N_p / N_s, \quad a_{pm} = N_p / N_m, \quad N_p = N_m \text{ için } L_{mp} = L_m, \quad I_{Lm} \ll I_g$$




$$V_c = \lambda \frac{V_g}{a}$$

$$0 < \lambda < 1/2$$



3/18/2023

100 W - 500 W

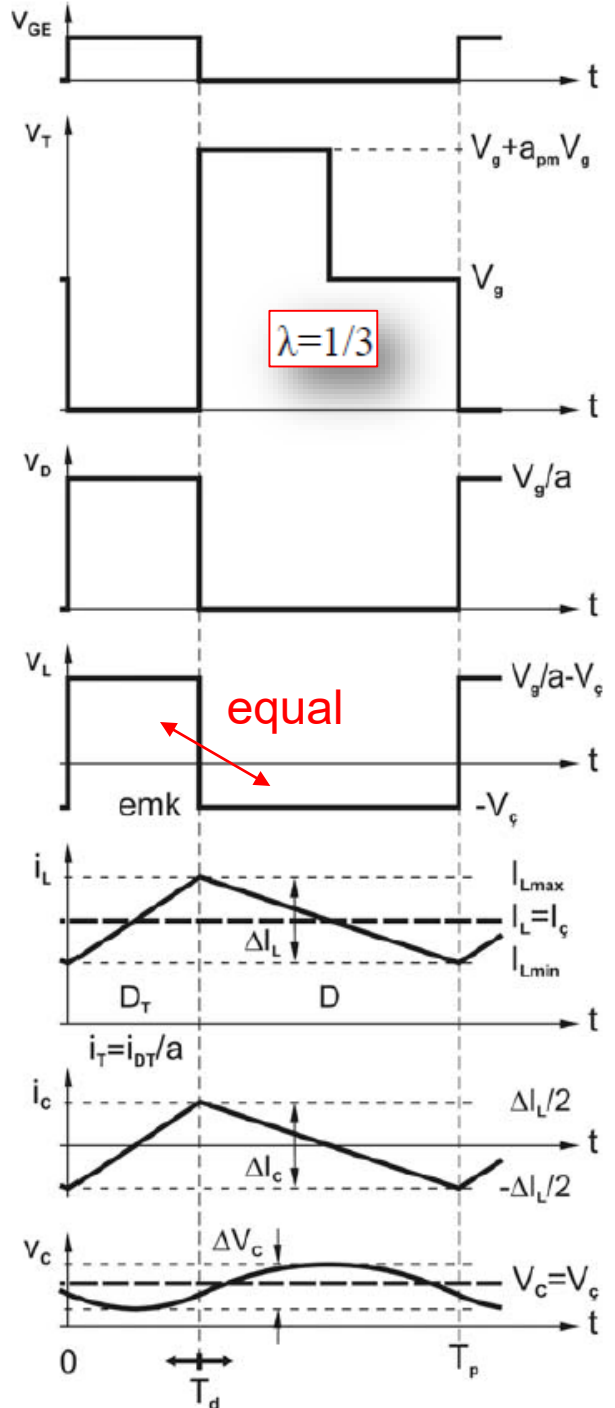

Flyback Converter

Buck-boost converter

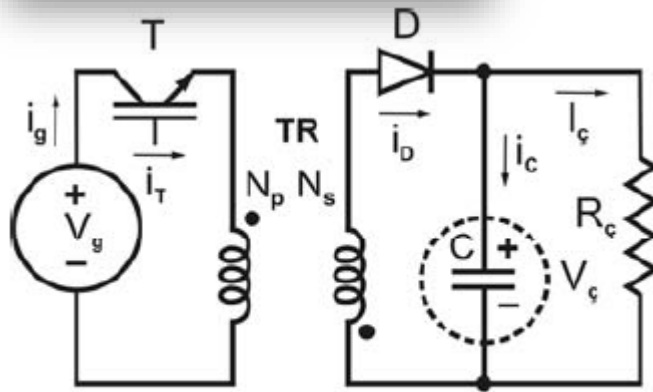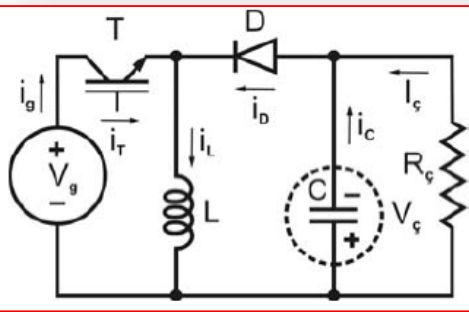


$$a = N_p / N_s, L_{mp} = L_p, L_{ms} = L_s, I_{Lmp} = I_g$$

$$V_c = \frac{\lambda}{1 - \lambda} \frac{V_g}{a}$$

In the flyback converter, the energy storage is the transformer itself, which is why a transformer with an air gap is needed.

The forward converter uses a transformer without an air gap, so an additional storage choke is needed. The forward converter is therefore somewhat more complex in design, but also achieves a higher efficiency.

3/18/2023

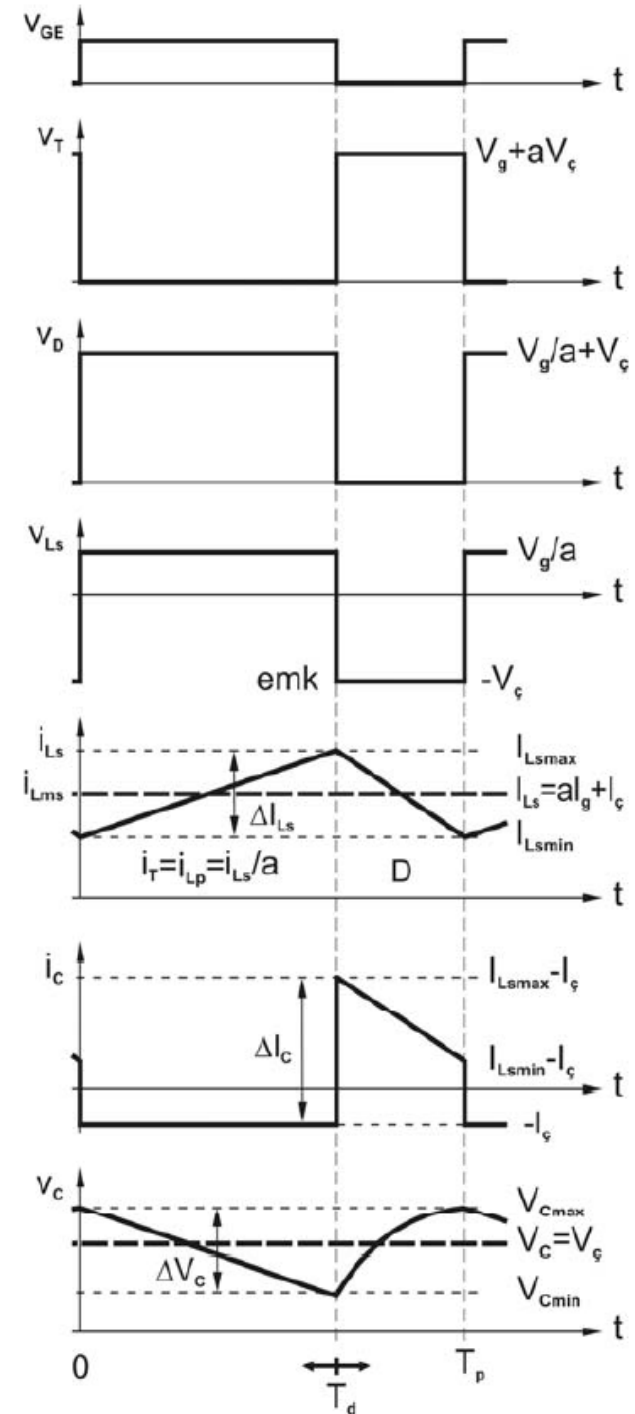

References



https://en.wikipedia.org/wiki/power_electronics

Prof. Mutlu Boztepe lecture notes

Güç Elektroniği, Prof. Dr. Hacı Bodur

Power Electronics, Muhammad H. Rashid

Power Electronics, Daniel W. Hart

Power Electronics, Dr M D Singh, Dr K B Khanchandani

Power Electronics, Soumitra Kumar Mandal

Power Electronics, Issa Batarseh, Ahmad Harb

Power Electronics, Branko L. Dokić, Branko Blanuša

Power Electronics, Ned Mohan

Basic Principles of Power Electronics, Klemens Heuman